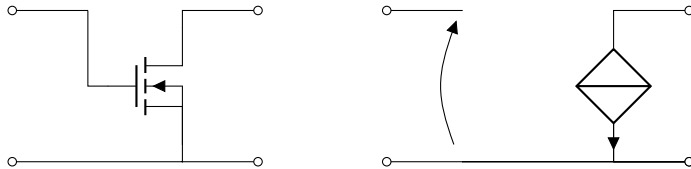


18 janvier 2019


1 Transistors

1.1 Alone



```
\begin{circuitikz} \draw
  (2.25, 1) node[nfet] (mos) {}
  (mos.D) -- (2.25, 2) to [short, -o](3.25, 2) node[anchor=west] {}
  ↪ %D
  (mos.S) -- (2.25, 0) to [short, -o](3.25, 0) node[anchor=west] {}
  ↪ %S
  (mos.B) -- (mos.S)
  (2.25,0) to [short, -o](0,0) node[anchor=west] {} %s
  (0,2) node[anchor=west]{}[short, o-] to (1,2) %G
  (1,2) -- (1,1) -- (mos.G)
;
\end{circuitikz}\hspace*{1cm}
\begin{circuitikz}\draw
  (0,0) node[anchor=west] {} %g
  to [short, o-] (1,0)
  to [open, v<={~}] (1,-2)
  to [short, -o] (4,-2)
  to [short, -o] (0,-2) node[anchor=west] {} %s
  (3,0) to [cI, i={~}] (3,-2)
  (3,-2) to [short, -o] (4,-2) node[anchor=west] {} %s
  (3,0) to [short, -o] (4,0)
  to node[anchor=west] {} (4,0) %d
;\end{circuitikz}
```

1.2 Alone with voltage and current

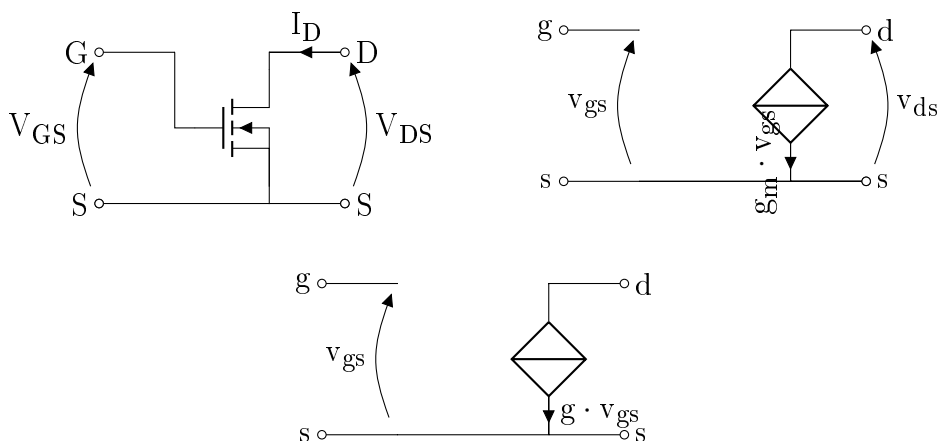

```
\begin{circuitikz} \draw
  (2.25, 1) node[nfet] (mos) {}
  (mos.D) -- (2.25, 2) to [short, -o, i<={~I_D$}](3.25, 2) node[anchor=west] {D}
  ↪ %D
```


```

(mos.S) -- (2.25, 0) to [short, -o](3.25, 0) node[anchor=west] {S}
↪ %S
(mos.B) -- (mos.S)
(2.25,0) to [short, -o](0,0) node[anchor=west] {S} %S
(0,2) node[anchor=west]{G}[short, o-] to (1,2) %G
(1,2) -- (1,1) -- (mos.G)
(0,0) [open,v^>=$V_{GS}$] to (0,2)
(3.25,0) [open,v>=$V_{DS}$] to (3.25,2)
;\end{circuitikz}\hspace*{1cm}
\begin{circuitikz}\draw
(0,0) node[anchor=west] {g} %g
to [short, o-] (1,0)
to [open, v<=$v_{gs}$] (1,-2)
to [short, -o] (4,-2)
to [short, -o] (0,-2) node[anchor=west] {s} %s
(3,0) to [cI, i_=\rotatebox{90}{$g_m\cdot v_{gs}$}] (3,-2)
(3,-2) to [short, -o] (4,-2) node[anchor=west] {s} %s
(3,0) to [short, -o] (4,0)
to node[anchor=west] {d} (4,0) %d
(4.0,-2) [open,v>=$v_{ds}$] to (4.0,0)
;\end{circuitikz}

\begin{circuitikz}\draw
(0,0) node[anchor=west] {g}
to [short, o-] (1,0)
to [open, v<=$v_{gs}$] (1,-2)
to [short, -o] (0,-2)
to (0,-2) node[anchor=west] {s}
(3,0) to [cI=$g\cdot v_{gs}$] (3,-2)
(3,-2) to [short, -o] (4,-2) node[anchor=west] {s}
(3,0) to [short, -o] (4,0)
to node[anchor=west] {d} (4,0)
(1,-2) -- (3,-2)
;\end{circuitikz}

```

1.3 Full common source

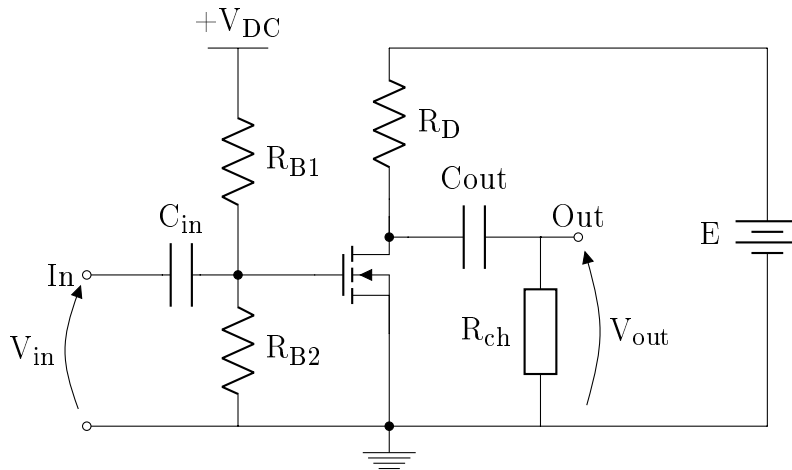

```

\begin{circuitikz}[scale=1]\draw
(0,1) to [short,o-] (9,1)
(4,6) to [short] (9,6)
(0,3) node[anchor=west] {In} to [short,o-] (1,3)
(0,3) node[anchor=south]{ } to [open, v_<=$V_{in}$] (0,1)
(1,3) to [C=$C_{in}$] (1.5,3)
(1.5,3) to [short,*] (2,3) node[anchor=south west]{ }

(2,6) node[anchor=south ] (alim) {$+V_{DC}$}
(1.6,6) -- (2.4,6) %bar under the label
(2,3) to [R, l_=$R_{B1}$] (2,6)

```


```

(2,3) to [R= $R_{B2}$ ](2,1)
(4,3) node[nfet] (mos) {}
(mos.G) to [short] (2,3)
(mos.D) to (4,4) to [R, l_= $R_D$ ] (4, 6)
(mos.D) to [short,-*](4,3.5) to [short] (4.25,3.5)
(mos.S) to [short] (4,1) % to [short, -o](2,0) node[anchor=west] {S}
(mos.S) -- (mos.B) %source to bulk connection

(4.25,3.5) node[anchor=south]{} to [C, l^= $C_{out}$ ] (6,3.5) to
↪ [short](6,3.5)node[anchor=south]{} to [short,-o](6.5,3.5)node [anchor=south]
↪ {Out}
(6,3.5) to [generic, l_= $R_{ch}$ ] (6,1)
(6.5,3.5) to [open,v^<= $V_{out}$ ] (6.5,1)
(9,6) to [battery, l_= $E$ ](9,1)
(4,1) node[circ]{}
(4,1) node[ground]{}
;\end{circuitikz}

```

1.4 Common source - Direct polarisation

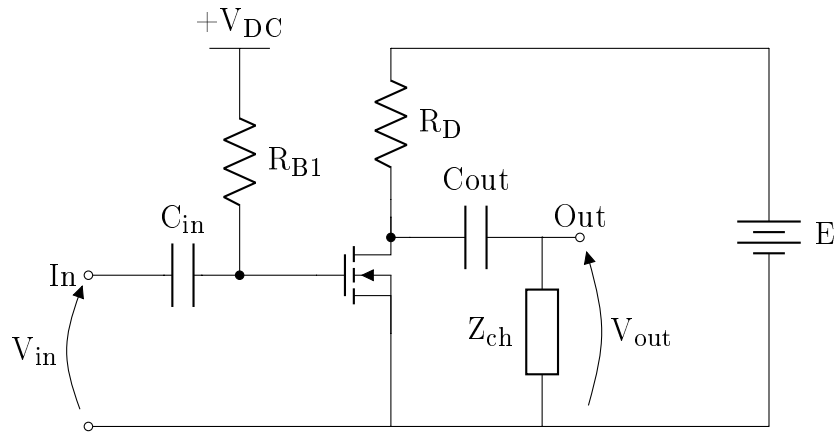


```

\begin{circuitikz}[scale=1]\draw
(0,1) to [short,o-] (9,1)
(4,6) to [short] (9,6)
(0,3) node[anchor=east] {In} to [short,o-] (1,3)
(0,3) to [open, v_<= $V_{in}$ ] (0,1)
(1,3) to [C= $C_{in}$ ] (1.5,3)
(1.5,3) to [short,-*] (2,3)
(2,6) node[anchor=south] (alim) { $+V_{DC}$ }
(1.6,6) -- (2.4,6) %bar under the label
(2,3) to [R, l_= $R_{B1}$ ] (2,6)
(4,3) node[nfet] (mos) {}
(mos.G) to [short] (2,3)
(mos.D) to (4,4) to [R, l_= $R_D$ ] (4, 6)
(mos.D) to [short,-*](4,3.5) to [short] (4.25,3.5)
(mos.S) to [short] (4,1) % to [short, -o](2,0) node[anchor=west] {S}
(mos.S) -- (mos.B) %source to bulk connection

(4.25,3.5) to [C, l^= $C_{out}$ ] (6,3.5) to [short](6,3.5) to [short,-o](6.5,3.5)node
↪ [anchor=south] {Out}
(6,3.5) to [generic, l_= $Z_{ch}$ ] (6,1)
(6.5,3.5) to [open,v^<= $V_{out}$ ] (6.5,1)
(9,6) to [battery, l= $E$ ](9,1)
;\end{circuitikz}

```


1.5 Common source - small signal

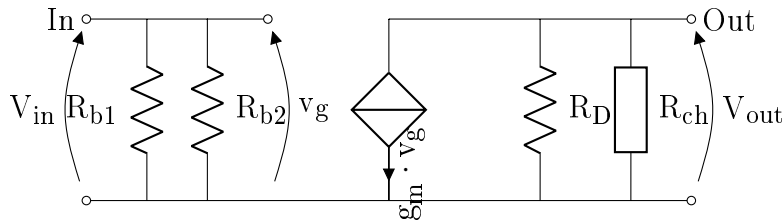

```
\begin{circuitikz}[scale=0.8]\draw
(1,0) to [short,o-o] (11,0)
(1,3) node[anchor=east] {In} to [short,o-] (1,3)
(1,3) to [open, v_<=$V_{in}$] (1,0)
(1,3) to [short] (3,3)
(2,3) to [R, l_=$R_{b1}$] (2,0)
(3,3) to [R=$R_{b2}$] (3,0)
(3,3) to [short,-o] (4,3) node [anchor=west] {}
(4,3) to [open, v_<=$v_g$] (4,0)
(6,3) to [cI=\rotatebox{90}{$g_m \cdot v_g$}] (6,0)
(8.5,0) to [R,l_=$R_D$] (8.5,3)
(10,3) to [generic, l=$R_{ch}$] (10,0)
(6,3) to [short,-o] (11,3) node [anchor=west] {Out}
(11,3) to [open, v_<=$V_{out}$] (11,0)
;\end{circuitikz}
```

2 Operational amplifiers

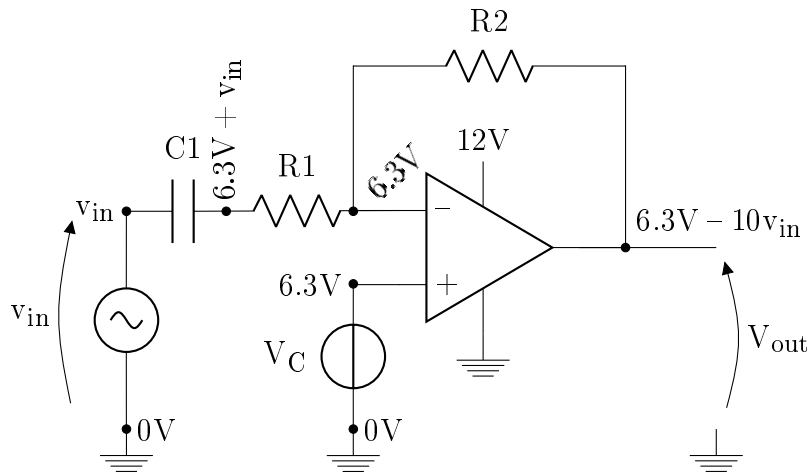2.1 Inverter with voltage and buffered offset



```
\begin{circuitikz} [scale=1.2]\draw
(0,0) node[op amp] (opamp) {}
(opamp.down) ++ (0,-0.5) node[ground]{} -- (opamp.down)
(opamp.up) ++ (0,.5) node[above] {12V} -- (opamp.up)
(opamp.-) -| (-1.5,2) to [R, l=$R2$] (1.5,2) |- (opamp.out)
(opamp.+) -| (-1.5,-0.4) to [european voltage source, l_=$V_{C}$,-*] (-1.5,-2)
-> node[ground] {}
(-4,-2) node[ground] {} to [sV,*-] (-4,0.4) |- ++(0.5,0) to [C,l=$C1$]
-> ++(0.25,0) to [R,l=$R1$] (opamp.-)
(-4,-2) node[anchor=west] {$0V$}
(-1.5,-2) node[anchor=west] {$0V$}
(-2.9,0.4) node[circ]{}
(-2.9,0.4) node[anchor=south]{\rotatebox{90}{$6.3V+v_{in}$}}
```

```

(-1.5,0.4) node[circ]{}
(-1.5,0.4) node[anchor=south west]{\rotatebox{42}{\color{red}$6.3V$}}
(-1.5,-0.4) node[circ]{}
(-1.5,-0.4) node[anchor=east]{\color{red}$6.3V$}
(1.5,0) node[circ]{}
(1.5,0) node[anchor=south west]{\color{red}$6.3V-10v_{in}$}
(opamp.out) to (2.5,0)
(2.5,-2) node[ground] {} to [open, v^>=\color{red}$V_{out}$] (2.5,0)
(-4.5,-2) to [open, v^>=\color{red}$v_{in}$] (-4.5,0.5)
(-4,0.4) node[anchor=east] {\color{red}$v_{in}$}
;\end{circuitikz}

```

Table des matières

1	Transistors	1
1.1	Alone	1
1.2	Alone with voltage and current	1
1.3	Full common source	2
1.4	Common source - Direct polarisation	3
1.5	Common source - small signal	4
2	Operational amplifiers	4
2.1	Inverter with voltage and buffered offset	4