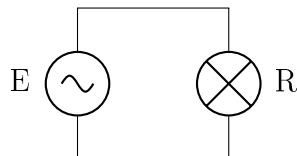


18 janvier 2019

1 Basic circuits


1.1 Voltage source and lamp



```
\begin{circuitikz}\draw
  (0,0) to [sinusoidal voltage source, l=$E$] (0,2)--(2,2) to [lamp, l=$R$] (2,0)
  \to --(0,0);
\end{circuitikz}
```


2 Filters

2.1 RLC - Out on RL

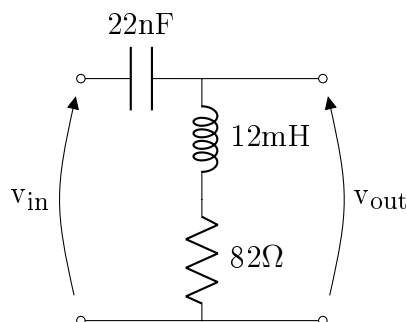

```
\begin{circuitikz}[scale=0.8]\draw
  (0,0) to [open, v^>=$v_{in}$,o-o] (0,4) to [C,l=$22\text{nF}$] (2,4) to [L,l=$12\text{mH}$]
  \to (2,2) to [R,l=$82\Omega$] (2,0) to [short](0,0)
  (2,4) -- (4,4) to [open, v^<=$v_{out}$,o-o] (4,0) -- (2,0);
\end{circuitikz}
```

2.2 RC high-pass

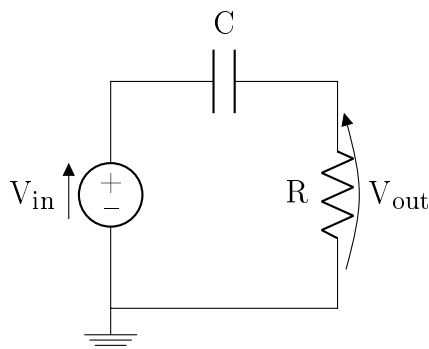


```

\begin{circuitikz} \draw
(0,0) node[ground]{}
to[american voltage source, v=$V_{in}$, invert] (0,3)
to[C, l=$C$] (3,3)
(3,0) to[R, l=$R$, v=$V_{out}$] (3,3)
(3,0)--(0,0);
\end{circuitikz}

```

2.3 RC high-pass with generator

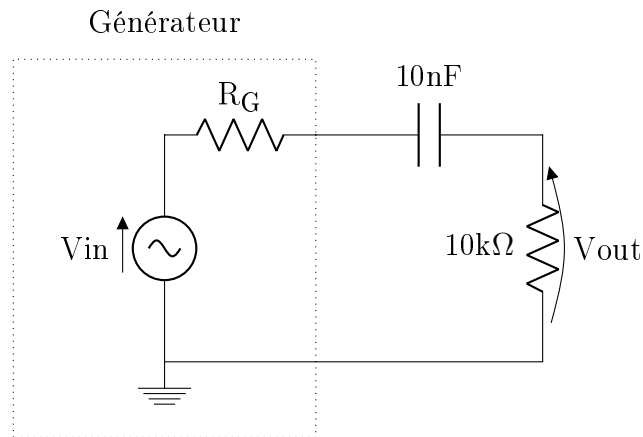


```

\begin{circuitikz} \draw
(0,0) node[ground]{}
to[sinusoidal voltage source, v=$V_{in}$] (0,3)
to[R, l=$R_G$] (2,3)
to[C, l=$10nF$] (5,3)
(5,0) to[R, l=$10k\Omega$, v=$V_{out}$] (5,3)
(5,0)--(0,0)
(0,4.5) node[] {Générateur};
\draw[dotted](-2,-1)--(-2,4)--(2,4)--(2,-1)--(-2,-1);
\end{circuitikz}

```

2.4 RLC - Out on C

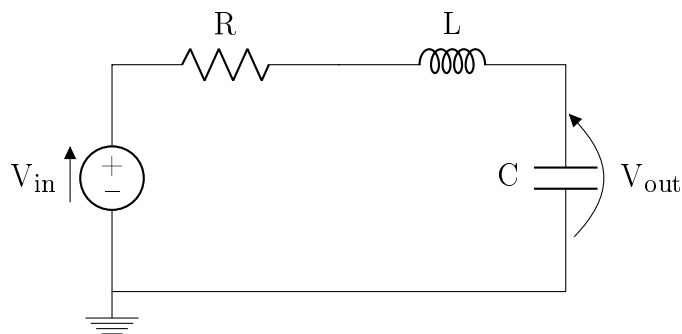


```

\begin{circuitikz} \draw
(0,0) node[ground]{}
to[american voltage source, v=$V_{in}$, invert] (0,3)
to[R, l=$R$] (3,3)
to[L, l=$L$] (6,3)
(6,0) to[C, l=$C$, v=$V_{out}$] (6,3)
(6,0)--(0,0);
\end{circuitikz}

```


2.5 RLC with generator - Out on C

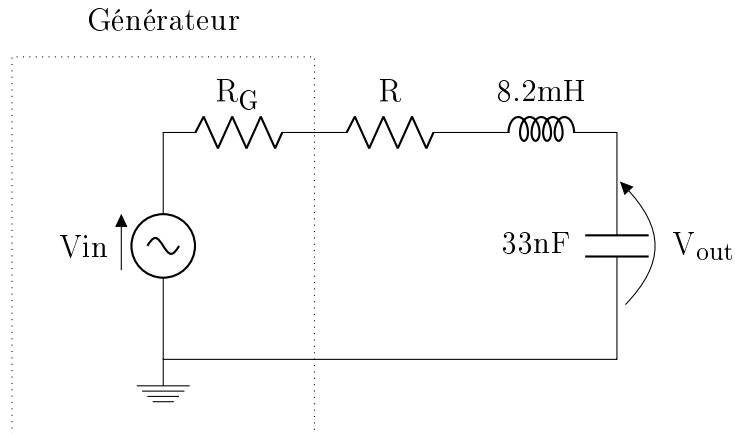

```
\begin{circuitikz} \draw
(0,0) node[ground]{}
to[sinusoidal voltage source, v=$V_{in}$] (0,3)
to[R, l=$R_G$] (2,3)
to[R, l=$R$] (4,3)
to[L, l=$8.2mH$] (6,3)
(6,0) to[C, l=$33nF$, v=$V_{out}$] (6,3)
(6,0)--(0,0)
(0,4.5) node[] {Générateur};
\draw[dotted](-2,-1)--(-2,4)--(2,4)--(2,-1)--(-2,-1);
\end{circuitikz}
```

3 Transistors

3.1 Alone

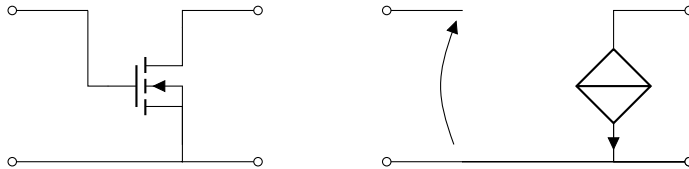


```
\begin{circuitikz} \draw
(2.25, 1) node[nfet] (mos) {}
(mos.D) -- (2.25, 2) to [short, -o](3.25, 2) node[anchor=west] {}
↪ %D
(mos.S) -- (2.25, 0) to [short, -o](3.25, 0) node[anchor=west] {}
↪ %S
(mos.B) -- (mos.S)
(2.25,0) to [short, -o](0,0) node[anchor=east] {} %s
(0,2) node[anchor=east]{}[short, o-] to (1,2) %g
(1,2) -- (1,1) -- (mos.G)
;
\end{circuitikz}\hspace*{1cm}
\begin{circuitikz}\draw
(0,0) node[anchor=east] {} %g
to [short, o-] (1,0)
to [open, v<={~}] (1,-2)
to [short, -o] (4,-2)
to [short, -o] (0,-2) node[anchor=east] {} %s
(3,0) to [cI, i={~}] (3,-2)
(3,-2) to [short, -o] (4,-2) node[anchor=west] {} %s
(3,0) to [short, -o] (4,0)
```

```

to node[anchor=west] {} (4,0) %d
;\end{circuitikz}

```

3.2 Alone with voltage and current

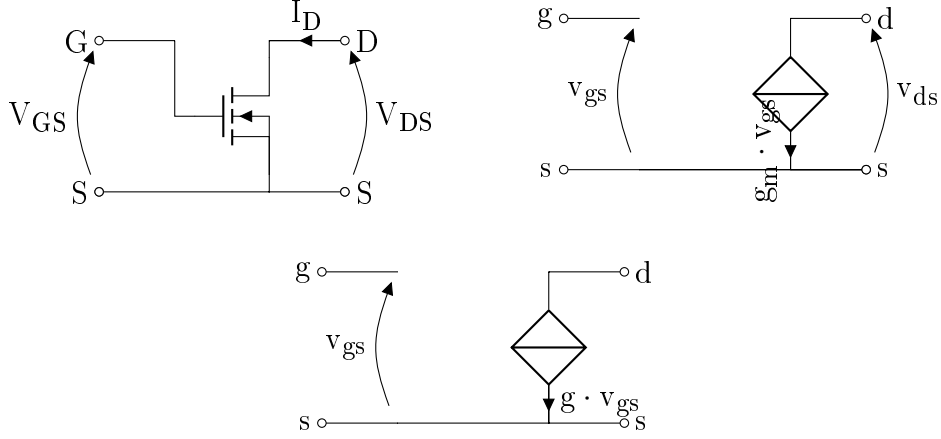


```

\begin{circuitikz} \draw
  (2.25, 1) node[nfet] (mos) {}
  (mos.D) -- (2.25, 2) to [short, -o, i<=I_D$(3.25, 2) node[anchor=west] {D}
  \curvearrowright %D
  (mos.S) -- (2.25, 0) to [short, -o](3.25, 0) node[anchor=west] {S}
  \curvearrowright %S
  (mos.B) -- (mos.S)
  (2.25,0) to [short, -o](0,0) node[anchor=west] {S} %S
  (0,2) node[anchor=west]{G}[short, o-] to (1,2) %G
  (1,2) -- (1,1) -- (mos.G)
  (0,0) [open,v^>=$V_{GS}$] to (0,2)
  (3.25,0) [open,v>=$V_{DS}$] to (3.25,2)
;\end{circuitikz}\hspace*{1cm}
\begin{circuitikz}\draw
  (0,0) node[anchor=west] {g} %g
  to [short, o-] (1,0)
  to [open, v<=$v_{gs}$] (1,-2)
  to [short, -o] (4,-2)
  to [short, -o] (0,-2) node[anchor=west] {s} %s
  (3,0) to [cI, i_=\rotatebox{90}{g_m\cdot v_{gs}}] (3,-2)
  (3,-2) to [short, -o] (4,-2) node[anchor=west] {s} %s
  (3,0) to [short, -o] (4,0)
  to node[anchor=west] {d} (4,0) %d
  (4.0,-2) [open,v>=$v_{ds}$] to (4.0,0)
;\end{circuitikz}

\begin{circuitikz}\draw
  (0,0) node[anchor=west] {g}
  to [short, o-] (1,0)
  to [open, v<=$v_{gs}$] (1,-2)
  to [short, -o] (0,-2)
  to (0,-2) node[anchor=west] {s}
  (3,0) to [cI=$g \cdot v_{gs}$] (3,-2)
  (3,-2) to [short, -o] (4,-2) node[anchor=west] {s}
  (3,0) to [short, -o] (4,0)
  to node[anchor=west] {d} (4,0)
  (1,-2) -- (3,-2)
;\end{circuitikz}

```

3.3 Full common source

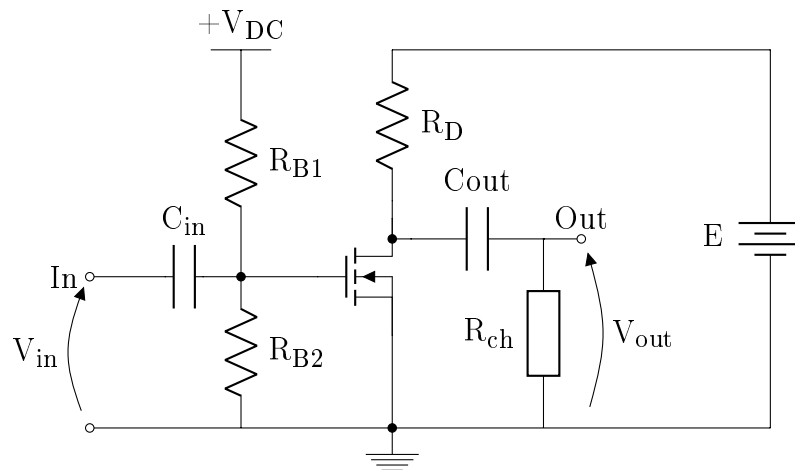

```


\begin{circuitikz}[scale=1]\draw
(0,1) to [short,o-] (9,1)
(4,6) to [short] (9,6)
(0,3) node[anchor=east] {In} to [short,o-] (1,3)
(0,3) node[anchor=south]{} to [open, v_<=$V_{in}$] (0,1)
(1,3) to [C=$C_{in}$] (1.5,3)
(1.5,3) to [short,-*] (2,3) node[anchor=south west]{}

(2,6) node[anchor=south] (alim) {$+V_{DC}$}
(1.6,6) -- (2.4,6) %bar under the label
(2,3) to [R, l_=$R_{B1}$] (2,6)
(2,3) to [R=$R_{B2}$] (2,1)
(4,3) node[nfet] (mos) {}
(mos.G) to [short] (2,3)
(mos.D) to (4,4) to [R, l_=$R_D$] (4, 6)
(mos.D) to [short,-*](4,3.5) to [short] (4.25,3.5)
(mos.S) to [short] (4,1) % to [short, -o](2,0) node[anchor=west] {S}
(mos.S) -- (mos.B) %source to bulk connection

(4.25,3.5) node[anchor=south]{} to [C, l^=$C_{out}$] (6,3.5) to
↪ [short](6,3.5)node[anchor=south]{} to [short,-o](6.5,3.5)node [anchor=south]
↪ {Out}
(6,3.5) to [generic, l_=$R_{ch}$] (6,1)
(6.5,3.5) to [open,v^<=$V_{out}$] (6.5,1)
(9,6) to [battery, l_=$E$] (9,1)
(4,1) node[circ]{}
(4,1) node[ground]{}
;\end{circuitikz}

```


3.4 Common source - Direct polarisation

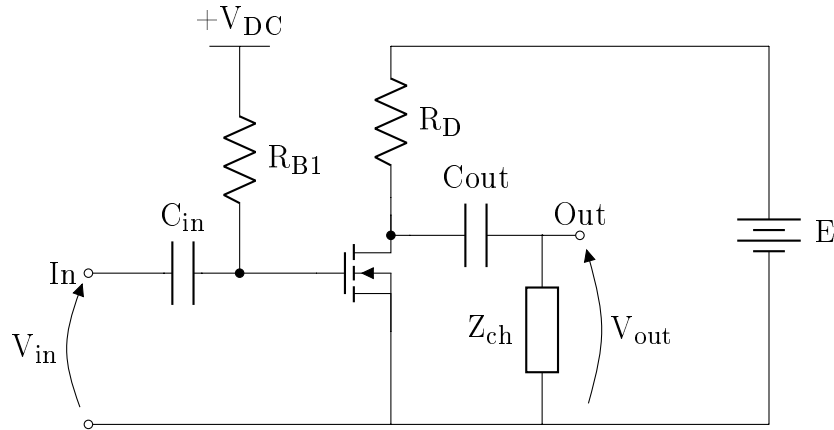

```
\begin{circuitikz}[scale=1]\draw
(0,1) to [short,o-] (9,1)
(4,6) to [short] (9,6)
(0,3) node[anchor=east] {In} to [short,o-] (1,3)
(0,3) to [open, v_<=$V_{in}$] (0,1)
(1,3) to [C=$C_{in}$] (1.5,3)
(1.5,3) to [short,-*] (2,3)
(2,6) node[anchor=south] (alim) {$+V_{DC}$}
(1.6,6) -- (2.4,6) %bar under the label
(2,3) to [R, l_=$R_{B1}$] (2,6)
(4,3) node[nfet] (mos) {}
(mos.G) to [short] (2,3)
(mos.D) to (4,4) to [R, l_=$R_D$] (4,6)
(mos.D) to [short,-*](4,3.5) to [short] (4.25,3.5)
(mos.S) to [short] (4,1) % to [short, -o](2,0) node[anchor=west] {S}
(mos.S) -- (mos.B) %source to bulk connection

(4.25,3.5) to [C, l^=$C_{out}$] (6,3.5) to [short](6,3.5) to [short,-o](6.5,3.5)node
↪ [anchor=south] {Out}
(6,3.5) to [generic, l_=$Z_{ch}$] (6,1)
(6.5,3.5) to [open,v_<=$V_{out}$] (6.5,1)
(9,6) to [battery, l=$E$](9,1)
;\end{circuitikz}
```

3.5 Common source - small signal

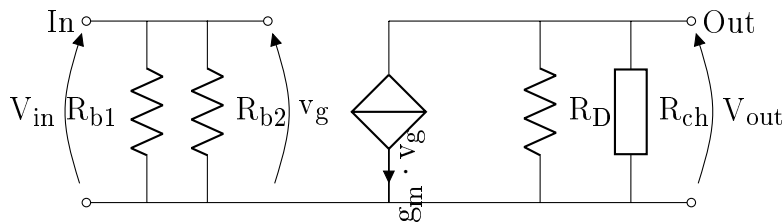

```
\begin{circuitikz}[scale=0.8]\draw
(1,0) to [short,o-o] (11,0)
(1,3) node[anchor=east] {In} to [short,o-] (1,3)
(1,3) to [open, v_<=$V_{in}$] (1,0)
(1,3) to [short] (3,3)
(2,3) to [R, l_=$R_{b1}$] (2,0)
(3,3) to [R=$R_{b2}$] (3,0)
(3,3) to [short,-o](4,3) node [anchor=west] {}
(4,3) to [open, v_<=$v_{g}$] (4,0)
(6,3) to [cI=\rotatebox{90}{$g_m \cdot v_{g}$}] (6,0)
```


```

(8.5,0) to [R,l_=$R_D$] (8.5,3)
(10,3) to [generic, l=$R_{ch}$] (10,0)
(6,3) to [short,-o] (11,3) node [anchor=west] {Out}
(11,3) to [open, v^<=$V_{out}$] (11,0)
;\end{circuitikz}

```

4 Operational amplifiers

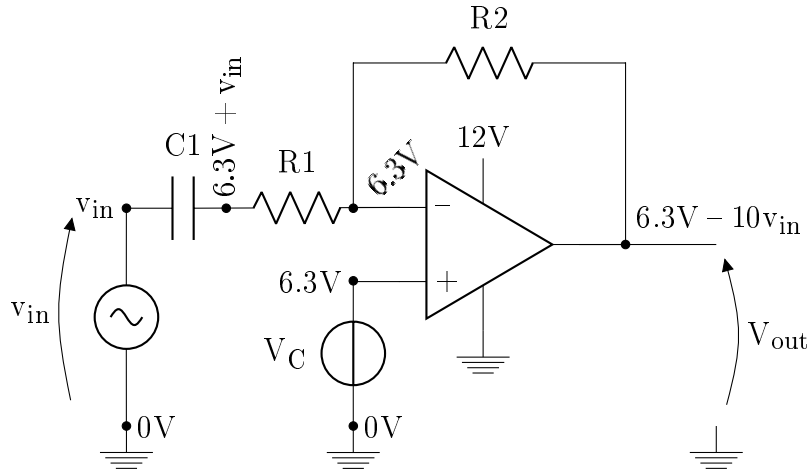
4.1 Inverter with voltage and buffered offset



```

\begin{circuitikz} [scale=1.2]\draw
(0,0) node[op amp] (opamp) {}
(opamp.down) ++ (0,-0.5) node[ground]{} -- (opamp.down)
(opamp.up) ++ (0,.5) node[above] {12V} -- (opamp.up)
(opamp.-) -| (-1.5,2) to [R, l=$R2$] (1.5,2) |- (opamp.out)
(opamp.+) -| (-1.5,-0.4) to [european voltage source, l_=$V_{C}$,-*] (-1.5,-2)
-> node[ground] {}
(-4,-2) node[ground] {} to [sV,*-] (-4,0.4) |- ++(0.5,0) to [C,l=$C1$]
-> ++(0.25,0) to [R,l=$R1$] (opamp.-)
(-4,-2) node[anchor=west] {$0V$}
(-1.5,-2) node[anchor=west] {$0V$}
(-2.9,0.4) node[circ]{}
(-2.9,0.4) node[anchor=south]{\rotatebox{90}{$6.3V+v_{in}$}}
(-1.5,0.4) node[circ]{}
(-1.5,0.4) node[anchor=south west]{\rotatebox{42}{$6.3V$}}
(-1.5,-0.4) node[circ]{}
(-1.5,-0.4) node[anchor=east]{$6.3V$}
(1.5,0) node[circ]{}
(1.5,0) node[anchor=south west]{$6.3V-10v_{in}$}
(opamp.out) to (2.5,0)
(2.5,-2) node[ground] {} to [open, v>=$V_{out}$] (2.5,0)
(-4.5,-2) to [open, v^>=$v_{in}$] (-4.5,0.5)
(-4,0.4) node[anchor=east] {$v_{in}$}
;\end{circuitikz}

```

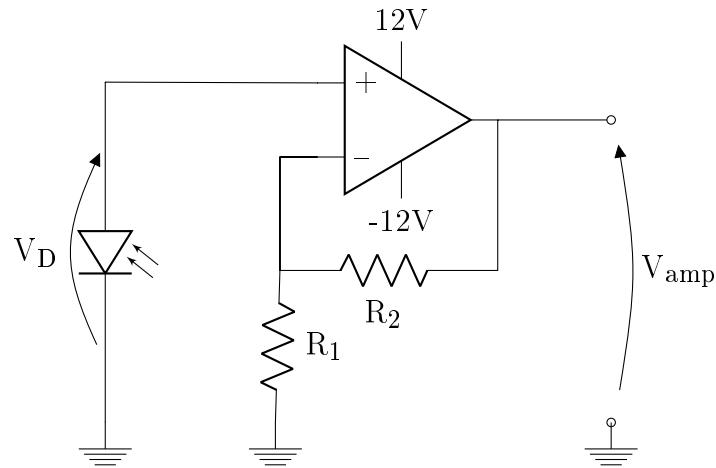


```

\begin{circuitikz}\draw
  (0,4.5) to [photodiode,v_<=$V_D$, ] (0,0) node [ground] {}
  (4,4) node[op amp, yscale=-1] (opamp) {}
  (opamp.down) ++ (0,+0.5) node[above] {12V} -- (opamp.down)
  (opamp.up) ++ (0,-0.5) node[below] {-12V} -- (opamp.up)
  (opamp.-) -| ++(-0.5,-1.5) to [R, l_=$R_2$] ++(2.75,0) -| (opamp.out)
  (opamp.-) -| ++(-0.5,-1.5) to [R, l=$R_1$] (2.25,0) node[ground] {}
  (opamp.+) to [short](0,4.5)
  (opamp.out) to [short] ++(1.5,0) node (A) {}
  to [open, v^<=$V_{amp}$, o-o] ++(0,-4) node [ground]{}
;
\end{circuitikz}

```

5 Diodes

5.1 Pulsed LED

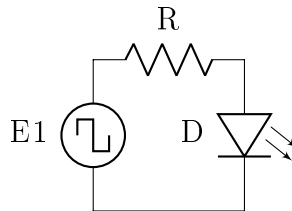


```

\begin{circuitikz}\draw
  (0,0) to [square voltage source, l=$E1$] (0,2) to [R, l=$R$] (2,2) to [led,
    ↗ l_=$D$] (2,0) --(0,0)
;
\end{circuitikz}

```



6 Graphs

6.1 Logarithmic axis

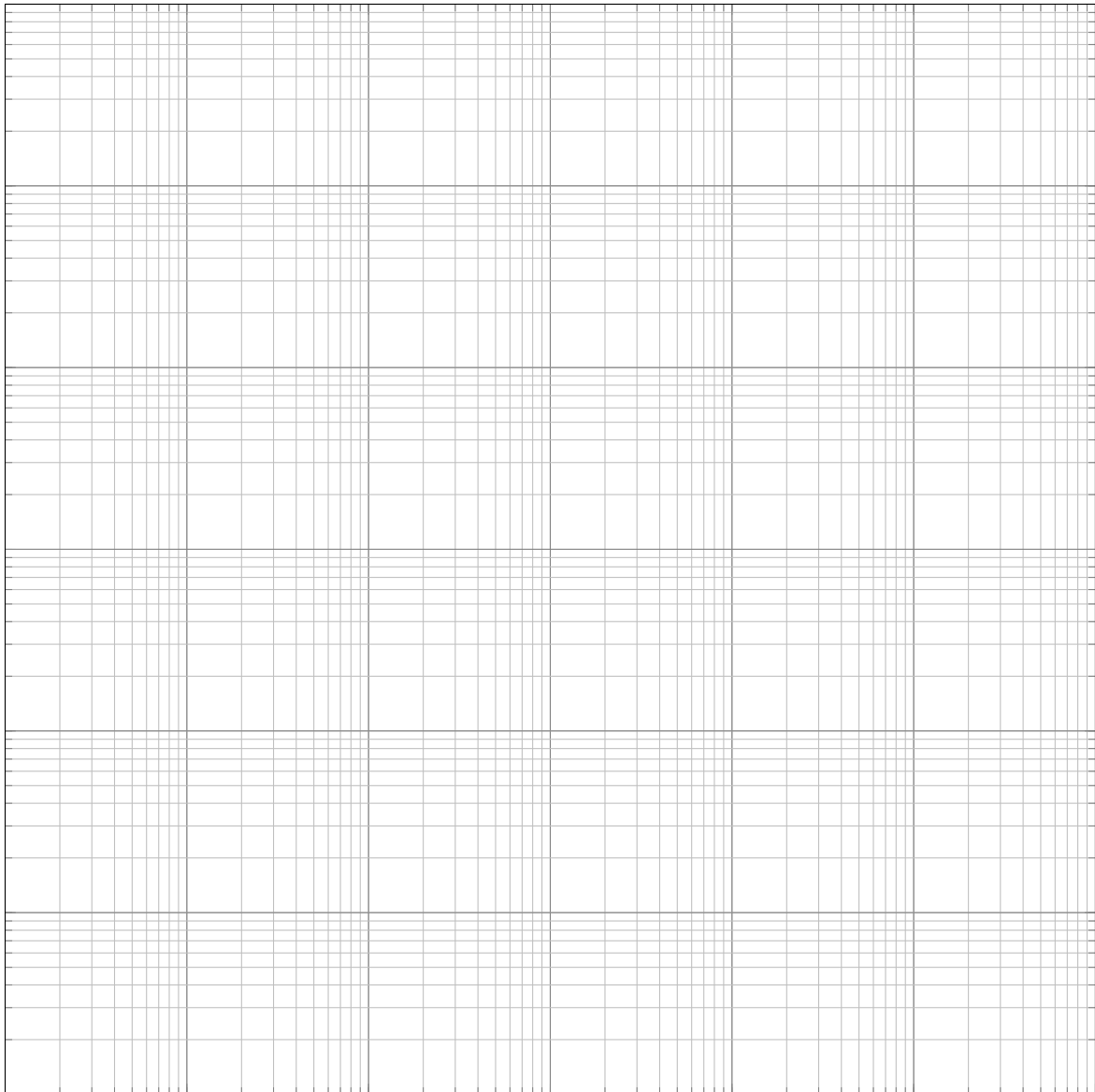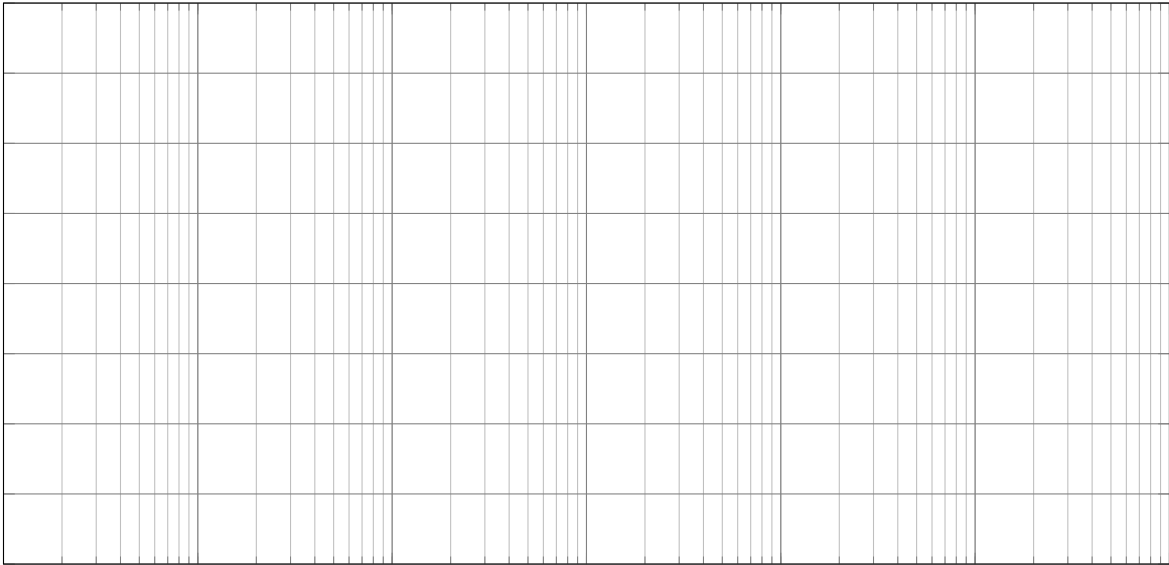

```
\begin{tikzpicture}
  \begin{loglogaxis}[
    xmin=1e-1, xmax=1e5,
    ymin=1e-1, ymax=1e5,
    yticklabels={,,},
    xticklabels={,,},
    grid=both,
    width=17cm,
    height=17cm,
    major grid style={black!50}
  ]
  \end{loglogaxis}
\end{tikzpicture}
```

6.2 Semi-logarithmic axis



```
\begin{tikzpicture}
  \begin{axis}[
    xmode=log,
    xmin=1e-1, xmax=1e5,
    ymin=1, ymax=9,
    yticklabels={,,},
    xticklabels={,,},
    grid=both,
    width=17cm,
    height=9cm,
    major grid style={black!50}
  ]
  \end{axis}
\end{tikzpicture}
```

Table des matières

1	Basic circuits	1
1.1	Voltage source and lamp	1
2	Filters	1
2.1	RLC - Out on RL	1
2.2	RC high-pass	1
2.3	RC high-pass with generator	2
2.4	RLC - Out on C	2
2.5	RLC with generator - Out on C	3
3	Transistors	3
3.1	Alone	3
3.2	Alone with voltage and current	4
3.3	Full common source	5
3.4	Common source - Direct polarisation	6
3.5	Common source - small signal	6
4	Operational amplifiers	7
4.1	Inverter with voltage and buffered offset	7
5	Diodes	8
5.1	Pulsed LED	8
6	Graphs	9
6.1	Logarithmic axis	9
6.2	Semi-logarithmic axis	10